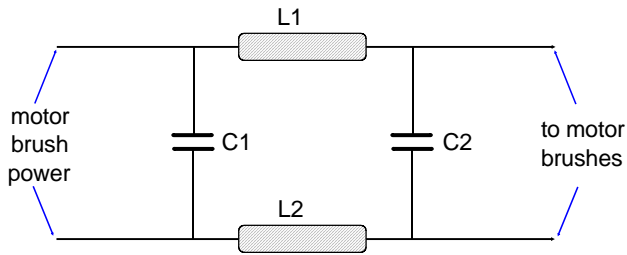
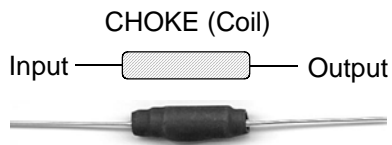


How to filter most motor noise from interfering with sound systems and other electronics. This can be used with DC and AC motors.



motor brush power is what was normally connected to the motor brushes but now gets connected to this filter.

- L1, L2 - motor chokes, item #702 for 1.5 amp motors, item #703 for up to 5 amp motors.
- C1, C2 - 4.7mfd non-polar capacitors, item #207. First try with only C2 in the circuit. If more filtering is necessary, then add C1. If more is needed place a second capacitor in parallel with C1 and C2.